

Seat No.	
-------------	--

SV - 445

Total No. of Pages : 2

S.E. (Electronics and Telecommunication) (Semester - IV) Examination,  
May - 2018

## ANALOG CIRCUITS - II

Sub. Code : 63466

Day and Date : Friday, 04 - 05 - 2018

Total Marks : 100

Time : 10.00 a.m. to 01.00 p.m.

- Instructions :
- 1) All questions are compulsory.
  - 2) Assume suitable data if required.
  - 3) Figure to right indicates full marks.

Q1) Attempt any three questions. [18]

- a) Derive the parameter equations such as  $R_i$ ,  $R_o$ ,  $A_v$  and  $A_i$  for multistage RC coupled amplifier.
- b) Explain operation of class AB push pull amplifier?
- c) What is harmonic distortion? Explain three-point method of calculating harmonic distortion of power amplifier.
- d) What is feedback? With the help of expressions explain advantages of negative feedback.

Q2) Attempt any two questions. [16]

- a) Design a two stage direct coupled amplifier for  $R_L = 5 \text{ k}\Omega$ ,  $V_{cc} = 10 \text{ V}$ ,  $R_s = 200 \Omega$  and frequency of operation = 7 Hz. Provide per stage gain greater than 11.
- b) Design class AB push pull amplifier for following specifications  
 $P_o = 600 \text{ mW}$ , Loud speaker impedance =  $6 \Omega$ ,  $V_{cc} = 15 \text{ V}$ .
- c) Design current series negative amplifier for following specifications,  
 $V_{cc} = 12 \text{ V}$ ,  $A_v = 25$ ,  $S = 9$ .

Q3) Attempt any two questions. [16]

- a) Design a two stage amplifier with per stage gain greater than 70 and lower 3dB frequency not more than 10 Hz. The output should be of 8V(p-p), Consider  $R_s = 300 \Omega$ ,  $V_{cc} = 12 \text{ V}$ ,  $S = 9$ .
- b) Design complimentary symmetry power amplifier to deliver a power of 2.2w to a load of  $8 \Omega$ . The lower 3dB cut-off frequency is 60 Hz.
- c) Derive the expression for  $R_{if}$ ,  $R_{of}$ ,  $A_{vf}$  and  $A_{if}$  for current series negative feedback.



Q4) Attempt any two.

[16]

- Design Hartely's oscillator for following data.  
 $F=10\text{KHz}$   $V_{o(p-p)} = 10\text{ V}$   $V_{cc} = 20\text{ V}$   $P_{D(max)} = 1\text{ W}$   
 $V_{CE} = 45\text{ V}$   $V_{ic(max)} = 1\text{ A}$   $h_{fe} = 200$   $h_{ic} = 4.5\text{ k}$ .
- Derive the expression for frequency of oscillation for Wein bridge oscillator.
- Design Wein bridge oscillator for following data  $F = 10\text{KHz}$   
 $V_{o(p-p)} = 10\text{ V}$   $V_{cc} = 20\text{ V}$   $P_{D(max)} = 1\text{ W}$   $V_{CE} = 45\text{ V}$   $V_{ic(max)} = 1\text{ A}$   $h_{fe} = 200$   
 $h_{ic} = 4.5\text{ k}$ .

Q5) Attempt any two.

[16]

- Derive expression for the time duration of astable multivibrator.
- Design the Schmitt trigger by using transistor. Assume following data :  
 $UTP = 2\text{ V}$   $LTP = 1\text{ V}$   $V_{cc} = 10\text{ V}$   $I_{csat} = 5\text{ mA}$   $V_{BEsat} = 0.7\text{ V}$   
 $h_{fe} = V_{CEsat} = 0.25\text{ V}$
- Design fixed bias bistable multivibrator. Using following  $h_{fe} = 100$ ,  
 $I_{Csat} = 10\text{ mA}$ ,  $V_{BEsat} = 0.7\text{ V}$ ,  $V_{CEsat} = 0.3\text{ V}$ ,  $V_{cc} = 12\text{ V}$ ,  $V_{BB} = -3\text{ V}$ ,  
 $OF = 2$ .

Q6) Write a short note any three.

[18]

- RC Phase shift oscillator
- Monostable multivibrator
- IC 723
- LM317 (Voltage Regulator)





SV - 446

Seat No.	
----------	--

Total No. of Pages : 2

S.E. (ETC) (Part - II) (Semester - IV) Examination, May - 2018

LINEAR INTEGRATED CIRCUITS (Revised)

Sub. Code : 63467

Day and Date : Monday, 07 - 05 - 2018

Total Marks : 100

Time : 10.00 a.m. to 01.00 p.m.

- Instructions :
- 1) All questions are compulsory.
  - 2) Figures to right indicate full marks.

**SECTION - I**

**Q1)** Attempt any two. [2 × 8 = 16]

- a) Draw and explain dual input, balanced output differential amplifier with DC analysis.
- b) Explain ideal characteristics of op-amp.
- c) Explain two circuits used for level shifting.

**Q2)** Attempt any two. [2 × 8 = 16]

- a) Derive Equation for gain, input resistance output resistance for closed loop inverting amplifier.
- b) Draw and explain closed loop differential amplifier using two op-amps.
- c) Discuss the frequency response for compensated and uncompensated op-amp.

**Q3)** Attempt any two. [2 × 9 = 18]

- a) Draw the circuit of V - I converter if the load is
  - i) Floating
  - ii) Grounded
- b) Draw and explain positive and negative peak detector using op-amp with waveforms.
- c) Draw and explain full wave rectifier circuit using op-amp with waveforms.



P.T.O.

SECTION - II

Q4) Attempt any two.

[2 × 8 = 16]

- a) Draw and explain working principle of all pass filter and derive expression for gain and phase shift between input and output.
- b) Draw and explain Narrow Band-Reject filter & design it for  $f_N = 60$  Hz.
- c) Design a second order HPF for cut off frequency of 1KHz. Draw a circuit diagram.

Q5) Attempt any two.

[2 × 8 = 16]

- a) Draw neat circuit diagram of RC phase shift oscillator and derive equation for frequency of oscillations.
- b) Draw and explain square wave generator using op-amp and derive equation for frequency of oscillations.
- c) Draw and explain the circuit diagram of Monostable multivibrator using op-amp and derive expression for pulse width.

Q6) Attempt any two.

[2 × 9 = 18]

- a) Define the terms
  - i) lock range
  - ii) capture range and
  - iii) pull in time
- b) Draw and explain the circuit diagram of Astable multivibrator using IC 555 and design Astable multivibrator using IC 555 with frequency 2kHz and duty cycle of 75%.
- c) Draw and explain the circuit diagram of Monostable multivibrator using IC 555 and derive expression for pulse width.

▽▽▽▽



Seat No.	
----------	--

**S.E. (Electronics & Telecommunication) (Part - II)****(Semester - IV) Examination, May - 2018****ELECTROMAGNETIC ENGINEERING****Sub. Code : 63469****Day and Date : Monday, 14 - 05 - 2018****Total Marks : 100****Time : 10.00 a.m. to 01.00 p.m.**

- Instructions :**
- 1) All questions are compulsory.
  - 2) Figures to the right indicate full marks.
  - 3) Assume suitable data if necessary.

**Q1) Solve any two :****[16]**

- a) Point charge of 120 nc are located at A(0, 0, 1) and B(0, 0, -1) in free space
  - i) Find E at (0.5, 0, 0)
  - ii) What single charge at the origin would provide the identical field strength.
- b) Transform cartesian coordinate system to spherical coordinate system.
- c) Given two charge distributions in free space : 0.2nc/m on the line  $z = 1$ ,  $y = 3$  and a point charge of 0.5nc at the origin. Find  $\vec{E}$  at point (2, 3, 4).

**Q2) Solve any two :****[16]**

- a) State and prove electric field intensity due to infinite sheet charge.
- b) A point charge 25nc is located in free space at p(2, -3, 5) and a perfectly conducting plane is at  $Z = 2$  find.
  - i) V at (3, 2, 4)
  - ii)  $\vec{E}$  at (3, 2, 4)
  - iii)  $\rho_s$  at (3, 2, 2)
- c) If  $V = x - y + xy + z$  (volts) find  $\vec{E}$  at (1, 2, 4) and the electrostatic energy stored in a cube of side 2m centered at origin.

**P.T.O.**

Q3) Solve any three :

[18]

- Explain applications of Gauss's law.
- Write short note on boundary condition for dielectric - dielectric interface.
- Explain method of images.
- Derive the equation for workdone in moving a point charge. Also explain conservative field.

Q4) Attempt any two of the following :

[2 × 8 = 16]

- Derive Magnetic field intensity on the axis of circular loop.
- Explain the concept of vector magnetic potential.
- Each of the three co-ordinate axis carries a filamentary current of 1A in  $\bar{a}_x$ ,  $\bar{a}_y$  &  $\bar{a}_z$  direction. Find  $\bar{H}$  at (2, 3, 4).

Q5) Attempt any two of the following :

[2 × 8 = 16]

- Derive maxwell's equations for time varying fields.
- For the space show that intrinsic impedance,  $\eta=120\pi$ .
- Calculate the intrinsic impedance  $\eta$ , the propagation constant  $\gamma$ , velocity  $v$  & skin depth for the given medium. Also check whether the medium is good conductor or not for which  $\sigma = 58\text{Ms/m}$ ,  $\mu_r = 1$  at frequency  $f=100\text{MHz}$ .

Q6) Attempt any two of the following :

[2 × 9 = 18]

- Explain smith chart and its applications.
- The characteristic impedance of a certain line is  $710 \angle -16^\circ$  when the frequency is 1KHz. At this frequency the attenuation 0.01 neper/Km & the phase function is 0.035 radians per km. Calculate the resistance, the leakage, the inductance & the capacitance per Km & velocity of propagation.
- A lossless transmission line of  $50\Omega$  is terminated in  $25+j50\Omega$ . Find using smith chart,
  - VSWR
  - Reflection coefficient
  - Impedance at  $0.3\lambda$  from load.





SV - 447

Total No. of Pages : 2

Seat No.	
----------	--

**S.E.(Electronics and Telecommunication) (Part-II) (Semester - IV)**

**Examination, May - 2018**

**DATA STRUCTURE (New)**

**Sub. Code : 63468**

**Day and Date : Friday, 11 - 05 - 2018**

**Total Marks : 100**

**Time : 10.00 a.m. to 01.00 p.m.**

- Instructions :**
- 1) All questions are compulsory.
  - 2) Figure to the right indicate full marks.


**SECTION - I**

**Q1) Solve any TWO from THREE [18]**

- a) What is stack? Write algorithm for push operation to save item on stack and explain it in brief.
- b) Write 'C' code for
  - i) Removing element from Queue
  - ii) Inserting element into Queue
- c) What is Data Structure? Discuss briefly different types of data structure.

**Q2) Solve any TWO from THREE [16]**

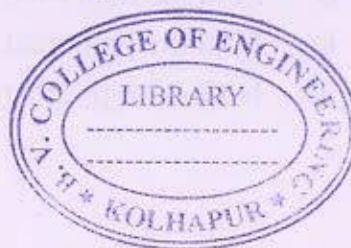- a) What is Linear search? Write algorithm for linear search in case of an array and explain its time complexity.
- b) Describe with 'C' code deletion of nodes from linked list
- c) Translate, by inspection, each infix expression to the corresponding postfix and prefix expression
  - i)  $(A+B)*D)/(E-F)$
  - ii)  $A+B/C*(D+E/F-G)+H$



**P.T.O**

Q3) Solve any TWO from THREE

[16]

- Write the C program for PUSH operation and POP operation
- What is time space trade off? Explain with example.
- What is Queue? Explain different types of queue.

### SECTION - II

Q4) Solve any TWO

[18]

- Write an algorithm for post order traversal using stacks
- Explain insertion in m-way search tree with proper example
- Explain construction of heap tree with example

Q5) Solve any TWO


[16]

- Explain binary tree with neat diagram and properties
- Explain traversing operation on a graph and its types
- Explain insertion of a node in AVL tree with different propositions

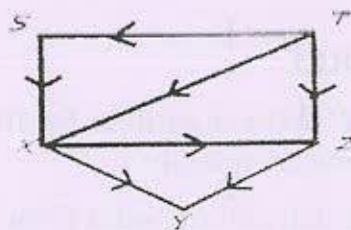Q6) Solve any TWO from THREE

[16]

- Write an algorithm for shortest path algorithm.
- Explain different collision resolution techniques.
- Consider graph G in the figure below, Suppose the nodes are stored in an array in a memory as follows X,Y,Z,S,T then



- Find the adjacency matrix A of G.
- Find the path matrix P of G.
- Is G strongly connected?





SV - 449

Seat No.	
-------------	--

Total No. of Pages : 2

**S.E. (Part - II) (ETC) (Semester - IV) Examination, May - 2018**

**ANALOG COMMUNICATION SYSTEM**

**Sub. Code : 63470**

**Day and Date : Wednesday, 16 - 05 - 2018**

**Total Marks : 100**

**Time : 10.00 a.m. to 01.00 p.m.**

- Instructions :**
- 1) All questions are compulsory.
  - 2) Figures to the right indicate full marks.
  - 3) Assume suitable data if necessary.

**SECTION - I**

**Q1) Solve any three.**

**[3 × 6 = 18]**

- a) Explain need of modulation
- b) An AM transmitter operating at carrier frequency of 1 MHz and modulating frequency of 5 KHZ and modulated at 60% depth delivers a carrier power of 6KW into 50 Ω load, Obtain power delivered to load ,total power of modulated signal in db & watt.
- c) Draw and explain high level DSBFC.
- d) Describe operation of third method of SSB.

**Q2) Solve any two.**

**[2 × 8 = 16]**

- a) Comment on pre-emphasis and de-emphasis used in FM.
- b) Compare AM with FM.
- c) Describe direct method of FM generation

**Q3) Solve any two.**

**[2 × 8 = 16]**

- a) Define receiver parameters Selectivity, Sensitivity, Fidelity, Dynamic range.
- b) Describe TRF receiver comment on limitations.
- c) Explain demodulation of SSB.



**P.T.O.**

**SECTION - II****Q4) Solve any two****[2 × 8 = 16]**

- a) Write note on FM Noise triangle.
- b) Explain Ratio detector.
- c) Explain with block diagram double conversion FM receiver.

**Q5) Solve any two****[2 × 8 = 16]**

- a) Explain flat top sampling also compare with natural sampling
- b) Explain thermal noise and partition noise
- c) Write note on classification of noise

**Q6) Solve any three****[3 × 6 = 18]**

- a) Draw and explain PPM modulator and demodulator.
- b) Compare PAM with PWM.
- c) Explain effect of aliasing in sampling.
- d) Explain PCM with block diagram.

▽▽▽▽



Seat	
No.	

SV - 442

Total No. of Pages : 2

**S.E. (Electronics & Telecommunication) (Semester - III)**

**Examination, April - 2018**

**ANALOG CIRCUITS - I**

**Sub. Code : 63461**

**Day and Date : Wednesday, 25 - 04 - 2018**

**Total Marks : 100**

**Time : 02.30 p.m. to 05.30 p.m.**

- Instructions :**
- 1) All questions are compulsory.
  - 2) Right to figure indicates full marks.
  - 3) Use data sheets
  - 4) Assume suitable data wherever necessary.

**SECTION-I**

**Q1) Solve any two : [16]**

- a) Explain working of high pass filter as a differentiator Design high pass filter for cutoff frequency of 6kHz.
- b) What is clamper circuit? Explain the operation of negative clamper in detail.
- c) Write short note on voltage tripler.

**Q2) Solve any two [16]**

- a) Explain HWR with resistive load Derive expressions for
  - i)  $V_{dc}$
  - ii)  $V_{rms}$
  - iii)  $r$
  - iv) Rectification efficiency ( $\eta$ )
- b) What is need of filter? explain with neat diagram & waveforms capacitor filter in detail.
- c) Design power supply using LC filter for following specifications.  
 $V_{dc} = 12v$ ,  $I_{dc} = 90 \text{ mA}$ ,  $r = 0.01$ .

**Q3) Solve any two : [18]**

- a) Explain working of zener shunt regulator and hence design it for  
 $V_o = 5.1v$ ,  $I_o = 50mA$ ,  $V_{in} = 7 \text{ to } 15 \text{ V}$ .
- b) Design feedback type series pass regulation should provide  $V_o = 9.4$ ,  
 $I_o = 80mA$ ,  $V_{in} = 15 \text{ to } 20v$  use transistor  $Q_1$  (controller) having  $h_{fe} = 40$   
 and transistor  $Q_2$  (error) having  $h_{fe} = 110$
- c) Explain different overload protection circuits used in voltage regulation.

**P.T.O.**



Q4) Attempt any two questions.

- Draw and explain hybrid equivalent circuit for CC configuration of transistor.
- Derive expression for  $A_v$ ,  $Y_i$ ,  $A_v$  and  $R_o$  of  $C_E$  amplifier in terms of h-parameter.
- Derive expression for lower 3dB frequency of CE amplifier by considering coupling capacitor  $[C_c]$ . Calculate  $C_c$  for  $R_1 = 12K\Omega$ ,  $R_2 = 6.8K\Omega$ ,  $h_{ie} = 4.5 K\Omega$ ,  $h_{fe} = 320$ ,  $R_s = 400\Omega$ .

Q5) Attempt any two questions.

[16]

- Draw and explain high frequency model for transistor. Derive expression for  $f_{\beta}$  and  $f_T$ . Consider  $R_L$ .
- Derive the expression for higher cut off frequency of R-C coupled amplifier considering square wave.
- Design single stage R-C coupled  $C_E$  amplifier  $V_{cc} = 12V$ ,  $h_{fe} = 150$ ,  $A_v = 60$ ,  $h_{ie} = 2.2K\Omega$ , frequency range 20kHz,  $S = 10$

Q6) Attempt any three question.

[18]

- Derive the expression for lower cut off frequency of R-C coupled amplifier considering square wave.
- Explain the transfer characteristics of n - channel JFET.
- Explain with circuit self bias for FET.
- For  $C_E$  amplifier has  $h_{fe} = 100$ ,  $h_{ie} = 2K\Omega$ ,  $h_{oe} = 50 \times 10^{-6}$ ,  $h_{re} = 2 \times 10^{-4}$ ,  $R_c = 2K\Omega$ ,  $R_L = 5.6K\Omega$ ,  $R_1 = 10 K\Omega$ ,  $R_2 = 4.7 K\Omega$ . Calculate  $A_v$ ,  $A_i$ ,  $Y_o$ .





Seat No.	
-------------	--

**S.E. (E.&TC) (Semester - III) Examination, April - 2018**

**TRANSDUCER & MEASUREMENT (Revised)**

**Sub. Code : 63464**

**Day and Date : Saturday, 28 - 04 - 2018**

**Total Marks : 100**

**Time : 02.30 p.m. to 05.30 p.m.**

**SECTION - I**

**Q1) Attempt any two:**

**[16]**

- Define transducer. Explain the various factors for the selection of transducer for a specific application.
- What is pressure transducer. Explain any one in detail.
- Explain signal conditioning system.

**Q2) Attempt any two:**

**[16]**

- Explain the electromagnetic flowmeter in detail.
- Explain the first order LPF and derive the expression for the cutoff frequency.
- Explain photo transistor in detail.

**Q3) Write short notes on (any three):**

**[18]**

- Active Band stop filter.
- Thermocouple
- Null & deflection type instruments.
- Successive approximation ADC

**SECTION - II**

**Q4) Answer any two:**

**[16]**

- Explain various types and sources of errors in measurement system
- With block schematic and waveforms, explain Integrating type Digital voltmeter.
- With block diagram explain Logic Analyzer.

**P.T.O.**



Q5) Answer any two:

[16]

- a) What is Attenuator? Explain types of Attenuator in detail.
- b) A schering bridge has  $3300\Omega$  in one arm and its opposite arm has capacitor value of  $0.47\text{ }\mu\text{f}$ . The arm to the right of resistor arm is having  $1500\Omega$  resistor shunt with  $0.33\text{ }\mu\text{f}$ . Capacitor. Opposite to this arm unknown components are connected. Find value of component & its dissipation factor. Assume  $f = 1000\text{ Hz}$ .
- c) Derive expression for Wien Bridge.

Q6) Write short notes (any three)

[18]

- a) CRO Probes
- b) De sauty's Bridge
- c) Spectrum Analyzer
- d) Digital multimeter





Seat No.	
----------	--

**S.E. (Electronics and Telecommunication) (Part - II)**  
**(Semester - III) Examination, April - 2018**  
**DIGITAL ELECTRONICS**  
**Sub. Code : 63462**

Day and Date : Thursday, 26 - 04 - 2018

Total Marks : 100

Time : 02.30 p.m. to 05.30 p.m.

- Instructions :
- 1) All questions are compulsory.
  - 2) Figures to the right indicate full marks.
  - 3) Assume appropriate data if needed.

**Q1) Solve any two of the following. [16]**

- a) Design and implement full adder.
- b) Design and implement one bit comparator.
- c) Give the specifications of digital IC's & explain propagation delay.

**Q2) Solve any two of the following. [16]**

- a) Design and implement 4 bit Binary to Gray code converter.
- b) Design 8:1 MUX using two 4:1 MUX.
- c) Design following logic function using 16: 1MUX with truth table  

$$F = \sum m(0,1,3,5,8,11,12,14,15)$$

**Q3) Solve any two of the following. [18]**

- a) Evaluate & minimize following expression using k-map  

$$F(ABCD) = \sum m(0,1,4,5,6,7,9,11,15) + d(10,14)$$
- b) Design & implement 4 bit adder/subtractor using IC 7483.
- c) Explain Demux/Decoder IC 74138.



P.T.O.

**Q4)** Solve any two of the following [16]

- a) Explain J-K flip-flop with truth table & circuit diagram & also explain race around condition.
- b) Design & implement 3 bit ripple counter.
- c) Explain serial In/ serial out shift register (SISO)

**Q5)** Solve any two of the following. [16]

- a) Differentiate between TTL & CMOS
- b) Draw & explain 4 bit synchronous up-counter.
- c) Give general classification of memories & explain any one in brief.

**Q6)** Solve any two of the following. [18]

- a) What is CMOS inverter? Explain with help of circuit diagram and input-output characteristics.
- b) Generate excitation tables for all the flip-flops.
- c) Explain Five-bit Johnson counters with timing diagram.






SV - 443

16) a) Derivation equation for characteristic impedance of  $\pi$  - network. [8]b) Design a  $m$  - derived high pass filter with a cut off frequency of 10kHz, design impedance of  $5\Omega$  and  $m = 0.4$  [8]

17) a) Explain a complete response of series R-L circuit for sinusoidal input. [8]

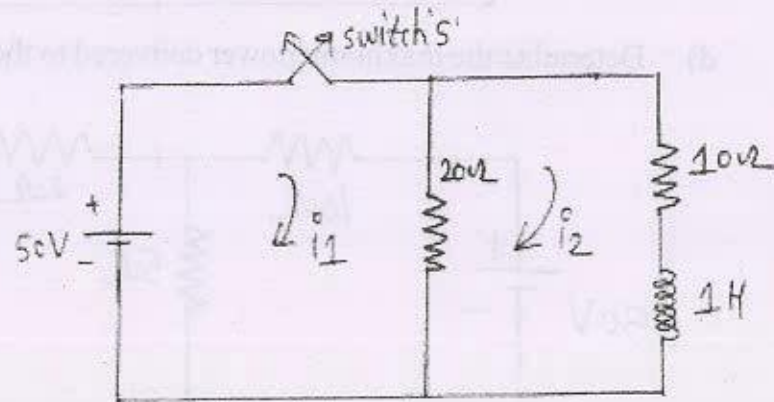b) In the circuit shown, obtain the equations for  $i_1(t)$  and  $i_2(t)$  when the switch 's' is closed at  $t = 0$  [8]

18) Solve any three.

a) Compare Series resonance and parallel resonance circuit. [6]

b) Explain Dc response of RLC series circuit. [6]

c) Design constant K-type low pass filter (both T and  $\pi$  sections) having a cutoff frequency of 2kHz to operate with a terminated load resistance of  $500\Omega$  [6]d) Design a Band Elimination filter having a design impedance of  $600\Omega$  and cut off frequencies  $f_1 = 2\text{kHz}$  and  $f_2 = 6\text{kHz}$ . [6]

iii

SV - 443

Total No. of Pages : 4

Seat  
No.

S.E. (Electronics and Telecommunication) (Semester - III)

Examination, April - 2018

NETWORK ANALYSIS (Revised)

Sub. Code : 63463

Day and Date : Friday, 27 - 04 - 2018


Total Marks : 100

Time : 02.30 p.m. to 05.30 p.m.


- Instructions :
- 1) Q. No. 4 from section - I and Q. No.8 from section - II is compulsory and solve any two questions from remaining three questions of each section
  - 2) Figures to the right indicate full marks.
  - 3) Assume suitable data wherever necessary.

SECTION - I

Q1) a) State and prove maximum power transfer theorem for D.C. Network. [8]

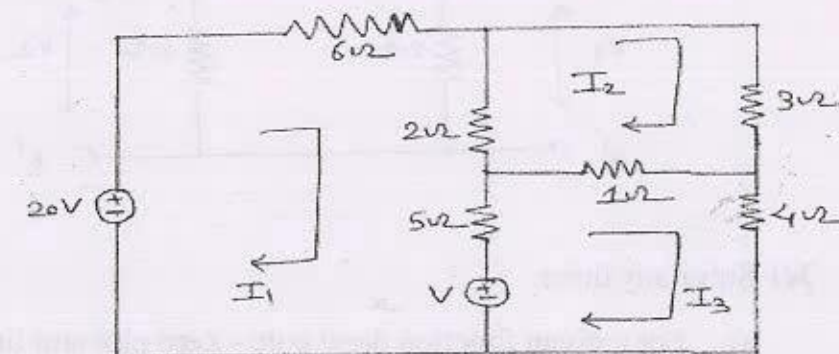b) Determine the voltage 'V' which causes the Current  $I_1$  to be zero. Use mesh analysis. [8]

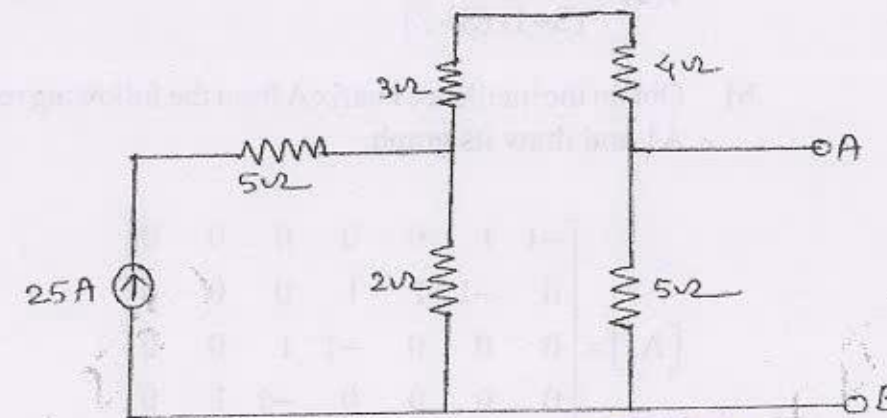Q2) a) Determine norton's equivalent circuit for the given circuit. [8]




P.T.O.






SV - 443

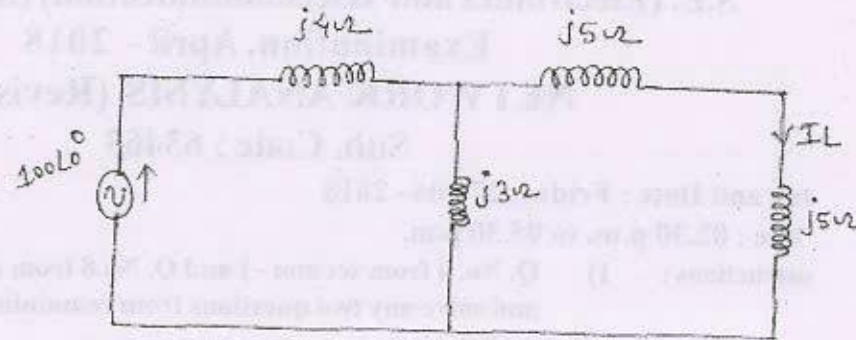- b) For the circuit shown, determine the load current using thevenin's theorem. [8]



- 23) a) Obtain ABCD parameters in terms of Y parameters for two port network. [8]

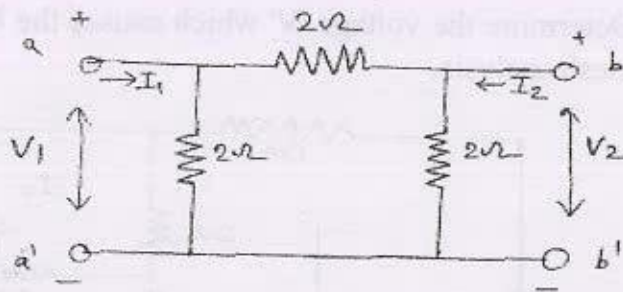- b) Find the transmission parameters for given circuit. [8]



- 24) Solve any three.

- a) For a given function draw pole - Zero plot and find  $i(t)$ . [6]


$$I(S) = \frac{4.5}{(S+1)(S+2)}$$

- b) Obtain the incidence matrix A from the following reduced incidence matrix  $A_1$  and draw its graph. [6]


$$[A_1] = \begin{bmatrix} -1 & 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & -1 & 1 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & -1 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & -1 & 1 & 0 \\ 0 & 0 & -1 & 0 & 0 & -1 & 1 \end{bmatrix}$$

SV - 443

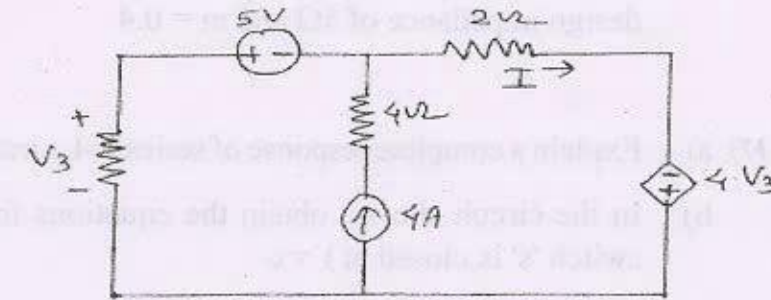- c) Determine the current through the  $2\Omega$  resistor using superposition theorem. [6]




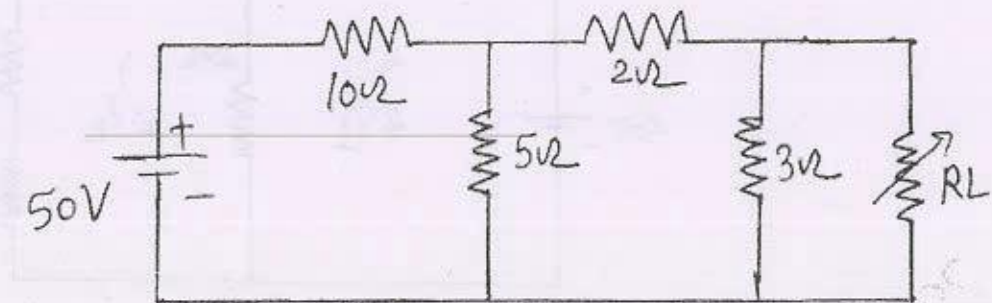- d) Determine the maximum power delivered to the load for given circuit. [6]



### SECTION - II

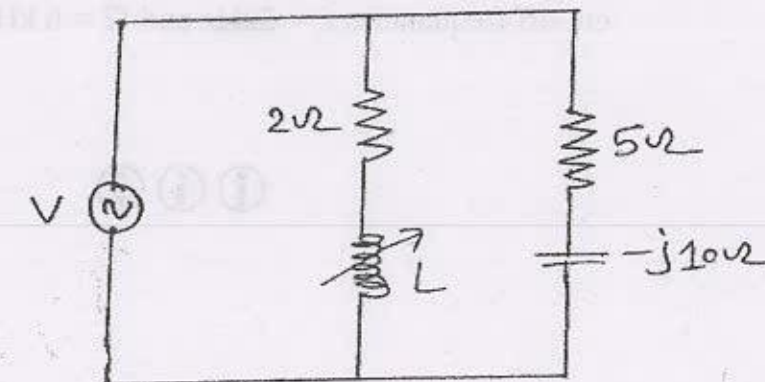- 25) a) Derive equation of resonant frequency for tank circuit. [8]  
b) Find the value of L for which the circuit shown, is resonant at a frequency of  $\omega = 500$  rad/sec. [8]





Seat No.	
----------	--

**S.E. (Electronics and Telecommunication Engineering) (Part - II)**  
**(Semester - III) Examination, April - 2018**  
**ENGINEERING MATHEMATICS - III**  
**Sub. Code : 63460**

Day and Date : Tuesday, 24 - 04 - 2018

Total Marks : 100

Time : 02.30 p.m. to 05.30 p.m.

- Instructions:
- 1) All questions are compulsory.
  - 2) Figures to the right indicate full marks.
  - 3) Use of non-programmable calculator is allowed.

**SECTION - I**

**Q1)** Solve any three of the following:

- a)  $(D^2 + 4D + 5)y = -2 \cosh x$  [6]
- b)  $(D^2 - 3D - 4)y = e^x \cos x$  [6]
- c)  $(D^3 - 2D + 4)y = 3x^2 - 5x + 2$  [6]
- d)  $\frac{d^2y}{dx^2} + \frac{dy}{dx} = \frac{1}{1+e^x}$  [6]

**Q2)** Attempt any two of the following:


- a) find the fourier series for,

$$f(x) = \begin{cases} -\pi, & -\pi < x < 0 \\ x, & 0 < x < \pi \end{cases}$$

Hence deduce that  $\frac{1}{1^2} + \frac{1}{3^2} + \frac{1}{5^2} + \dots = \frac{\pi^2}{8}$  [8]

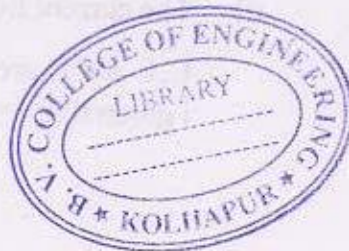- b) Obtain a fourier expression of  $f(x) = 2x - x^2$  in interval  $(0, 2)$ . [8]
- c) Obtain half range sine series for [8]

$$\begin{aligned} f(x) &= \frac{\pi}{3}, & 0 \leq x \leq \frac{\pi}{3} \\ &= 0, & \frac{\pi}{3} \leq x \leq \frac{2\pi}{3} \\ &= -\frac{\pi}{3}, & \frac{2\pi}{3} \leq x \leq \pi \end{aligned}$$



P.T.O.

3) Attempt any two of the following:

a) Find Fourier trans form of

$$f(x) = 1 - x^2, |x| \leq 1$$

$$= 0, \text{ otherwise}$$

[8]

b) Find fourier sine and cosine transforms of the function  $f(x) = x^{n-1}$ . [8]

c) i) find  $f(x)$  satisfying following integral equation. [5]

$$\int_0^\infty f(x) \sin sx dx = \begin{cases} 1, & 0 \leq s \leq 1 \\ 2, & 1 \leq s \leq 2 \\ 0, & s \geq 2 \end{cases}$$

ii) if  $f(x) = \sin px$ , where  $0 \leq x \leq \pi$  and  $p$  is a positive integer, show that finite Fourier sine transform of  $f(x)$ ,  $F_s(n) = 0$  if  $n \neq p$ . [3]

### SECTION - II

4) Attempt any three of the following:

a) Find  $L \left\{ \int_0^t \frac{e^{-u} \sin 2u}{u} du \right\}$ . [6]

b) Find the Laplace transform of

$$f(t) = t, \quad 0 < t \leq a$$

$$= 2a - t, \quad a < t < 2a$$

$$\text{where } f(t) = f(t + 2a).$$

[6]

c) Evaluate  $\int_0^\infty t e^{-3t} J_0(4t) dt$ , given that  $L\{J_0(t)\} = \frac{1}{\sqrt{s^2 + 1}}$ . [6]

d) The current flowing in an electrical circuit is given by  $Ri + L \frac{di}{dt} = E$  where  $E, L$  and  $R$  are constants. Use laplace transform to solve the equation for  $i$  given that  $i = 0$  when  $t = 0$  [6]

5) Attempt any two of the following:

a) i) By using definition, find the Z-transform of  $\{f(k)\}$ , where [4]

$$f(k) = 5^k, k < 0$$

$$= 3^k, k \geq 0$$

ii) Find the z-transform of  $k^2 e^{k0}$  [4]

b) Show that  $Z\{\cosh \alpha k\} = \frac{z(z - \cosh \alpha)}{z^2 - 2z \cosh \alpha + 1}, k \geq 0$ . [8]

c) Find the inverse Z- transform of  $\frac{1}{(z-3)(z-2)}$ , for

i)  $2 < |z| < 3$ ,

ii)  $|z| > 3$ . [8]

6) Attempt any two of the following:

a) Find the directional derivative of  $f = xy^2 + yz^3$  at the point  $(2, -1, 1)$  in the direction of normal to the surface  $x \log z - y^2 = -4$  at  $(-1, 2, 1)$ . [8]

b) If  $\vec{a}$  is a constant vector and  $\vec{r} = xi + yj + zk, r = |\vec{r}|$  then [3]

i) Prove that  $\nabla(\vec{a} \cdot \vec{r}) = \vec{a}$

ii) Evaluate  $\nabla^2 e^{r^2}$  [5]

c) Show that the following vector field is irrotational and find the corresponding scalar potential. Also show that it is not solenoidal. [8]

$$\vec{F} = (ye^y \cos z)i + (xe^y \cos z)j - (e^y \sin z)k$$

