

Seat No.	
-------------	--

**S.E. (Electronics & Telecommunication) (Semester - III)**  
**Examination, May - 2019**  
**ANALOG CIRCUITS - I**  
**Sub. Code : 63461**

Day and Date : Thursday, 02 - 05 - 2019  
Time : 10.00 a.m. to 1.00 p.m.

Total Marks : 100

- Instructions :
- 1) All questions are compulsory.
  - 2) Right to figure indicates full marks.
  - 3) Use data sheets.
  - 4) Assume suitable data wherever necessary.

**Q1) Solve any two. [16]**

- a) Explain working of low pass filter as an integrator. Design low pass filter for cutoff frequency of 10KHz.
- b) What is clipper circuits? Explain diode series clipper with its transfer characteristics.
- c) Write short note on voltage Doubler.

**Q2) Solve any two. [16]**

- a) Explain BWR working with suitable diagrams. Derive expression for ripple factor, when capacitor filter is used.
- b) Explain with suitable diagram L filter & derive its ripple factor.
- c) Design power supply using capacitor filter for  $V_{dc} = 9V$ ,  $I_{dc} = 50mA$ ,  $r = 0.02$ .

**Q3) Solve any two. [18]**

- a) Design series pass transistor for following specifications  $V_o = 10.2V$ ,  $V_{in} = 15$  to  $20V$ ,  $I_o = 90mA$ ,  $h_{fe1} = 40$   $h_{fe2} = 110$ .
- b) Explain working of transistorised shunt regulator & then design it for  $V_{in} = 10$  to  $15V$ ,  $V_o = 6V$ ,  $I_o = 50mA$  use transistor having  $h_{fe} = 40$ .
- c) Explain the use of pre - regulator & write its design steps with the help of one example.



**P.T.O.**

Q4) Attempt any two questions.

[16]

- Draw and explain hybrid equivalent circuit for CB configuration of transistor.
- Derive expression for  $A_i$ ,  $Y_i$ ,  $A_v$  and  $R_o$  of  $C_E$  amplifier in terms of h-parameter.
- Derive expression for lower 3dB frequency of  $C_E$  amplifier by considering coupling capacitor  $[C_c]$ . Calculate  $C_c$  for  $R_1 = 10K\Omega$ ,  $R_2 = 4.7K\Omega$ ,  $h_{ie} = 3.8K\Omega$ ,  $h_{fe} = 100$ ,  $R_s = 500\Omega$ .

Q5) Attempt any two questions.

[16]

- Draw and explain high frequency model for transistor. Derive expression for  $f_B$  consider short circuit load.
- Derive the expression for higher cut off frequency of R-C coupled amplifier considering square wave.
- Design single stage R-C coupled  $C_E$  amplifier  $V_{CC} = 15V$ ,  $h_{fe} = 50$ ,  $A_v = 70$ ,  $h_{ie} = 3.2K\Omega$ , frequency range 10Hz to 20 kHz,  $S = 10$ .

Q6) Attempt any three questions.

[18]

- Derive the expression for lower cut off frequency of R-C coupled amplifier considering square wave.
- Explain the transfer characteristics of p-channel enhancement MOSFET.
- Explain with circuit voltage divider bias for FET.
- For  $C_E$  amplifier has  $h_{fe} = 50$ ,  $h_{ie} = 2.2K\Omega$ ,  $h_{oe} = 50 \times 10^{-6}$ ,  $h_{re} = 2 \times 10^{-4}$ ,  $R_c = 2K\Omega$ ,  $R_L = 5K\Omega$ ,  $R_1 = 12 K\Omega$ ,  $R_2 = 4.7K\Omega$ . Calculate  $A_v$ ,  $A_i$ ,  $Y_o$ .





SV-444

Total No. of Pages : 2

Seat No.	
----------	--

**S.E. (ETC) (Part - II) (Semester - IV)**  
**Examination, May - 2019**  
**ANALOG COMMUNICATION SYSTEM**  
**Sub. Code: 63470**

Day and Date : Friday, 24- 05 - 2019

Total Marks : 100

Time : 2.30 p.m. to 5.30 p.m.

- Instructions :
- 1) All questions are compulsory.
  - 2) Assume suitable data, if required.
  - 3) Figures to the right indicate full marks.

**SECTION - I**

**Q1) Solve any three :**

**[3×6]**

- a) Draw and explain Trapezoidal patterns for AM.
- b) Draw and explain frequency spectrum and phase representation of AM wave.
- c) A carrier wave frequency of 10Mhz and peak value of 10V is applied and amplitude modulated by a 5Khz sine wave of amplitude 6V. Determine modulation index and sideband frequencies.
- d) Describe operation of phase shift method of SSB.

**Q2) Solve any two :**

**[2×8]**

- a) Explain concept of angle modulation with respect to FM.
- b) Comment on pre-emphasis and de-emphasis used in FM.
- c) Write note on indirect method of FM generation.

**Q3) Solve any Two:**

**[2×8]**

- a) Explain methods of tracking.
- b) Explain effect of AGC with characteristics
- c) Write note on image frequency and double spotting.



**P.T.O.**

**SECTION - II****Q4) Solve any two :****[2×8]**

- a) Explain PLL-FM demodulator.
- b) Explain foster seeley discriminator.
- c) Explain in brief about noise figure, noise temperature, noise bandwidth, SNR.

**Q5) Solve any two :****[2×8]**

- a) Explain shot noise, thermal noise, avalanche noise, burst noise.
- b) Write note on flat top sampling.
- c) Write note on classification of noise.

**Q6) Solve any three****[3×6]**

- a) Explain PWM applications.
- b) Compare PAM with PWM.
- c) State and prove sampling theorem.
- d) Explain PCM transmitter.



SV-441

Total No. of Pages : 2

Seat No.	
----------	--

**S.E. (ETC) (Part - II) (Semester - IV) (Revised)**

**Examination, May -2019**

**LINEAR INTERGRATED CIRCUITS**

**Sub. Code : 63467**

**Day and Date : Thursday, 16 - 05 - 2019**

**Total Marks : 100**

**Time : 2.30 p.m. to 5.30 p.m.**

- Instructions :**
- 1) All questions are compulsory.
  - 2) Figures to the right indicates full marks.

**SECTION - I**

**Q1) Attempt any Two.**

**[2×8=16]**

- a) Draw AC equivalent circuit for DIBO-DA. Derive expression for  $R_i$  and  $R_o$ .
- b) Explain any four ideal and practical parameters of Op amp.
- c) With neat circuit diagram explain Instrumentation Amplifier using three op amp. Derive the expression for voltage gain for the same.

**Q2) Attempt any two.**

**[2×8=16]**

- a) Discuss any two methods of frequency compensation used in op amp.
- b) Explain open loop and closed loop configuration of op amp.
- c) Draw and explain peak detector in details.

**Q3) Write short notes on any three.**

**[3×6=18]**

- a) IC CA3140
- b) Thermal Drift
- c) Current mirror circuits
- d) Sample & Hold Circuits



**P.T.O.**



SECTION - II

Q4) Attempt any two.

[2×8=16]

- a) With neat circuit diagram explain Wide Band Reject Filter with its frequency response.
- b) Design second order low pass butterworth filter with higher cut off frequency of 2KHz. Draw the design circuit diagram and sketch its frequency response. Assume  $C = 0.01 \mu\text{f}$  and pass band gain = 1.586.
- c) With neat diagram explain Timer IC 555.

Q5) Attempt any two.

[2×8=16]

- a) With neat circuit diagram explain Hartley and Colpitts oscillator using Op amp.
- b) Explain triangular wave generator with waveform.
- c) Explain with neat diagram and waveform use of IC 555 as monostable multivibrator.

Q6) Write short notes on any three.

[3×6=18]

- a) IC OP 177 op amp
- b) IC 565 PLL
- c) RC phase shift oscillator
- d) Chebyshev filter

\* \* \*

Seat No.	
----------	--

## S.E. (E &amp; TC) (Part - II) (Semester - IV)

Examination, May - 2019

## ANALOG CIRCUITS - II

Sub. Code: 63466

Day and Date : Tuesday, 14-05-2019

Total Marks : 100

Time : 2.30 p.m. to 5.30 p.m.

- Instructions :
- 1) All questions are compulsory.
  - 2) Assume suitable data, if required.
  - 3) Figures to the right indicate full marks.

SECTION - I (A)

Q1) Attempt any two :

[16]

- a) Design two stage direct amplifier with transistor specification  $Q_1$  and  $Q_2$ ,  $h_{fe} = 100$ ,  $I_{C(max)} = 100mA$ ,  $V_{CE(max)} = 30V$ ,  $V_{O(p-p)} = 5V$ ,  $R_L = 10k\Omega$ ,  $V_{CC} = 24V$ ,  $s = 5$
- b) Derive the parameter equations such as  $R_i$ ,  $R_o$ ,  $A_v$  and  $A_i$  for voltage series negative feedback.
- c) Design current series negative amplifier for following specifications :  $V_{CC} = 12V$ ,  $A_v = 30$ ,  $S = 10$ , use transistor BC147A.

Q2) Attempt any two :

[16]

- a) Design two stage common emitter amplifier to provide the following specification.  
 $V_{CC} = 10V$ ,  $V_O = 3V$  (rms),  $AVF \geq 100$ ,  $R_S = 600\Omega$ ,  $R_L = 1k\Omega$ ,  $f = 20Hz-20kHz$ , use transistor BC147B
- b) Design class AB push-pull amplifier for following specifications :  
 $P_o = 400mW$ , loud speaker impedance =  $6\Omega$ ,  $V_{CC} = 12V$
- c) Design class A push-pull amplifier for following specifications :  
 $P_o = 500mW$ , loud speaker impedance =  $8\Omega$ ,  $V_{CC} = 12V$



P.T.O.



Q3) Write note on any three

[18]

- 3 point method of calculating harmonic distortion of power amplifier.
- Complementary symmetry power amplifier
- Types of negative feedback
- Classification of Power Amplifiers

### SECTION - II (B)

Q4) Attempt any two :

[16]

- Derive the expression for frequency of oscillation for Wein Bridge Oscillator.
- Design Hartley's Oscillator with following data  $V_o = 6V$  (p-p),  $F_o = 2MHz$ ,  $S = 9$ . Transistor Data,  $PD = 0.2 W$ ,  $V_{CE} (max) = 40V$ ,  $h_{fe} = 110$ ,  $h_{ie} = 2.7K\Omega$ ,  $I_C (max.) = 0.1A$
- Design RC phase shift oscillator for following data,  $F_o = 2.5KHz$ ,  $I_C (sat.) = 4.5mA$ ,  $h_{fe} = 50$ ,  $h_{ie} = 4.5K\Omega$ ,  $S = 10$ .

Q5) Attempt any two :


[16]

- Design astable multivibrator for symmetric square wave with following data, Frequency = 500Hz,  $V_o = 12V$ ,  $h_{fe}(min) = 50$ ,  $V_{BE}(sat.) = V_{CE}(sat.) = 0V$ ,  $I_C (sat.) = 6mA$ .
- Design power supply using LM 317 for following data  $V_O = 8$  to  $10V$  at  $100mA$  current, and Input voltage in the range of  $20V$  to  $24V$ .
- Design Monostable multivibrator for following data,  $T_P = 2.5ms$ ,  $V_{CC} = 10V$ ,  $V_{BB} = -2V$ ,  $V_{CE} (sat.) = 0.7V$ ,  $I_C (sat.) = 5mA$ ,  $C_1 = 0.3\mu F$ ,  $h_{fe}(min) = 40$ .

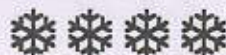Q6) Write note on any three

[18]

- IC 723.
- Barkhausen's criteria.
- Schmitt Trigger.
- Transistor switching parameters.





SV - 437

Total No. of Pages : 2

Seat No.	
-------------	--

**S.E. (Electronics & Telecommunication) (Part - I)**  
**(Semester - III) Examination, May - 2019**  
**DIGITAL ELECTRONICS**  
**Sub. Code : 63462**

**Day and Date : Saturday, 04 - 05 - 2019**  
**Time : 10.00 a.m. to 1.00 p.m.**

**Total Marks : 100**

- Instructions :**
- 1) All questions are compulsory.
  - 2) Figures to the right indicate full marks.
  - 3) Assume appropriate data if needed.

**Q1) Solve any two of the following. [16]**

- a) Design and implement half adder with truth table.
- b) Design and implement one bit comparator.
- c) Give the specifications of digital IC's & explain propagation delay.

**Q2) Solve any two of the following. [16]**

- a) Design and implement 4 bit Binary to Gray code converter.
- b) Design 8:1 MUX using two 4:1 MUX.
- c) Design following logic function using 16:1MUX with truth table  
$$F = \sum m(0,1,4,8,9,12,13,14).$$

**Q3) Solve any two of the following. [18]**

- a) Evaluate & minimize following expression using k-map  
$$F(ABCD) = \sum m(0,1,4,5,6,7,9,11,15) + d(10,14).$$
- b) Design & implement 4 bit comparator using IC7485.
- c) Explain multiplexer IC 74151.



**P.T.O.**

**Q4) Attempt any three.**

**[18]**

- a) With suitable logic diagram and truth table explain SR flip flop with preset and clear inputs.
- b) Explain serial in serial out 4-bit shift register. Draw waveforms also.
- c) Write excitation table for SR, D and JK flip flop.
- d) Explain 3-bit ripple down counter with suitable state diagram and truth table.

**Q5) Attempt any two.**

**[16]**

- a) Explain effect of clock skew and clock jitter on synchronous designs.
- b) Explain sequence detector with suitable example.
- c) Differentiate between Mealy & Moore machine.

**Q6) Attempt any two.**

**[16]**

- a) Explain classification of memories in detail.
- b) Realize JK flip flop using SR flip flop.
- c) Explain Static and Dynamic RAM cell.





SV - 443

Total No. of Pages : 3

Seat No.	
----------	--

**S.E. (ETC) (Semester - IV) Examination, May - 2019**  
**ELECTROMAGNETICS ENGINEERING**

**Sub. Code : 63469**

**Day and Date : Wednesday, 22 - 05 - 2019**

**Total Marks : 100**

**Time : 2.30 p.m. to 5.30 p.m.**

- Instructions :**
- 1) All Questions are compulsory.
  - 2) Neat diagrams must be drawn wherever necessary.
  - 3) Make suitable assumptions if necessary and state it clearly.

**SECTION-I**

**Q1) Solve any two.**


**[2×8=16]**

- a) A point charge  $Q_1 = 2 \text{ mC}$  is located in free space at  $P_1(-3, 7, 4)$  while  $Q_2 = 5 \text{ mC}$  is at  $P_2(2, 4, -1)$ . Find  $F_2$  &  $F_1$ .
- b) A uniform line charge,  $P_1 = 25 \text{ nC/m}$  lies on the line  $X = -3, Z = 4$  in free space. Find  $E$  in Cartesian components at Origin
- c) Find the gradient of the function  $A$  given  $A = \cosh xyz$ .

**Q2) Solve any two.**

**[2×8=16]**

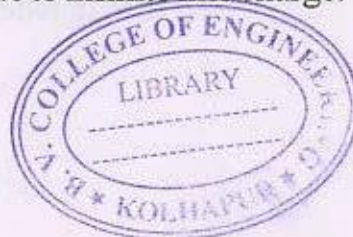- a) Evaluate work done in bringing a charge of  $\mu\text{C}$  from origin to  $P(2, -1, 4)$  through field  $E = 2xyz a_x + x^2z a_y + x^2y a_z$  (V/m) through the line path, straight line segments  $(0, 0, 0)$  to  $(2, 0, 0)$  to  $(2, -1, 0)$  to  $(2, -1, 4)$ .
- b) Explain electric flux density  $D$  for point charge, line charge and surface charge.
- c) Evaluate Electric field intensity due to infinite line charge.



**P.T.O.**



5) Solve any three.

[3×6=18]

- What is polarization in dielectric?
- Explain the Cylindrical coordinate system.
- Write a note on boundary condition for dielectric - dielectric interface.
- Explain method of image for line charge.

**SECTION-II**

4) Solve any two.

[2×8=16]

- Derive Maxwell's equation in point form.
- State and explain Stoke's Theorem in Cartesian, Cylindrical and spherical co-ordinate system.
- A plane wave travelling in air is normally incident on a block of a paraffin with  $\epsilon_r = 2.2$ . Find  $\Gamma_R$  and  $\Gamma_T$

5) Solve any two.

[2×8=16]

- A plane electromagnetic wave travelling in the +z direction in an unbounded lossless dielectric medium  $\epsilon_r=3$ ,  $\mu=1$  has peak electric intensity E of 6V/m. Find
  - The velocity of wave
  - The intrinsic impedance of the wave
  - The peak value of the magnetic field intensity H.
- Estimate the incremental field  $dH_2$  at point  $P_2$  caused by a source at  $P_1$  of  $I_1 dL_1$   
 $2\pi a_z - mt$ , given  $P_1(4,0,0)$  &  $P_2(0,3,0)$
- Derive magnetic field intensity due to infinite long straight filament.

6) Solve any three.

[3×6=18]

- Derive transmission line equation.
- State and explain wavelength, velocity of propagation and group velocity.
- A lossless transmission line is 80 cm long and operates at a frequency of 600 MHz. The line parameters are  $L = 0.25 \mu\text{H}/\text{m}$  and  $C = 100 \text{ pF}/\text{m}$ . Find the characteristic impedance, the phase constant and the phase velocity.
- An infinite long current filament is placed along z-axis. The magnetic field intensity at point P (3, 4, 0) is  $I_0 (-0.8a_x + 0.6a_y) \text{ A/m}$ . Find the current through the filament.

■ ■ ■



Seat No.	
----------	--

**S.E. (Electronics and Telecommunication Engineering)  
(Part - II) (Semester - III) Examination, April - 2019  
ENGINEERING MATHEMATICS - III**

**Sub. Code: 63460**

**Day and Date : Friday, 26 - 04 - 2019**

**Total Marks : 100**

**Time : 10.00 a.m. to 1.00 p.m.**

- Instructions :**
- 1) All questions are compulsory.
  - 2) Figures to the right indicate full marks.
  - 3) Use of non-programmable calculator is allowed.

**SECTION-I**

**Q1) Solve any three of the following.**

- a)  $(2D^2 + 5D - 3)y = \cos x$ . [6]
- b)  $(D^2 - 3D + 2)y = 5xe^x$ . [6]
- c)  $x^2 \frac{d^2 y}{dx^2} + x \frac{dy}{dx} = x^2 + 5$ . [6]
- d)  $(2D^2 + 5D)y = 3x^2 + 2x + 1$  [6]

**Q2) Solve any two of the following.** [8]

- a) Find Fourier series for  $f(x) = x^2$  in  $(0, 2\pi)$  Hence deduce that  

$$\frac{\pi^2}{3} = -\left\{ \frac{1}{1^2} + \frac{1}{2^2} + \frac{1}{3^2} + \dots \right\}$$
 [8]
- b) Find Fourier series for  $f(x) = e^{-x}$  in the interval  $(0, 2)$  [8]
- c) Obtain half range sine series for  $f(x) = \cos x$  in the interval  $(0, \pi)$ . [8]



**P.T.O.**

Q3) Attempt any two of the following.

- a) Find Fourier Transform of  $f(x) = \begin{cases} \frac{1}{2} & -1 \leq x \leq 1 \\ 0 & \text{otherwise} \end{cases}$  [8]
- b) Find Fourier Cosine Transform of  $f(x) = e^{-x}$  and find  $f(x)$  by using inverse Cosine Fourier transform. [8]
- c) Find finite Fourier Cosine Transform and its inverse of  $f(x) = 2x$  in  $0 < x < 4$ . [8]

**SECTION-II**

Q4) Attempt any three of the following.

[8]

- a) Find the Laplace transform of the periodic function  $f(t) = \frac{kt}{T}, 0 < t < T, f(t+T) = f(t)$ .
- b) Find the Laplace transform of  $\sin \sqrt{t}$ , hence find Laplace transform of  $\frac{\cos \sqrt{t}}{2\sqrt{t}}$ .
- c) Find the inverse Laplace transform of  $\frac{s+4}{(s^2+4)s(s-1)}$ .
- d) Using Laplace transform, solve  $(D^2+2D+5)y = e^{-t} \sin t$  where  $y(0) = 0$   $y'(0) = 1$ .

Q5) Attempt any two of the following.

[16]

- a) Find the Z-transform of  $\sin(3k+5), k \geq 0$ .
- b) Find the Z-transform of the following functions
- i)  $f(k) = 3(2^k) - 4(3^k), k \geq 0$
- ii)  $f(k) = a^{|k|}$
- c) Find the inverse Z-transform of  $\frac{2z^2 - 10z + 13}{(z-3)^2(z-2)}, 2 < |z| < 3$ .

[16]

Q6) Attempt any two of the following.

- a) A vector field  $\vec{F}$  is given by  $\vec{F} = (y \sin z - \sin x)i + (x \sin z + 2yz)j + (xy \cos z + y^2)k$ . Prove that it is irrotational and hence find its scalar potential.
- b) Find the constants  $a$  and  $b$  so that the surface  $ax^2 - 2byz = (a+4)x$  will be orthogonal to the surface  $4x^2y + z^3 = 4$  at  $(1, -1, 2)$ .
- c) Show that  $\nabla \left[ \frac{(\vec{a} \cdot \vec{r})}{r^n} \right] = \frac{\vec{a}}{r^n} - \frac{n(\vec{a} \cdot \vec{r})\vec{r}}{r^{n+2}}$ , Where  $\vec{r} = xi + yj + zk$  and  $\vec{a} = a_1i + a_2j + a_3k$ .





Seat No.	
----------	--

**S.E. (ETC) (Part - II (Semester - III))**  
**Examination, May - 2019**  
**NETWORK ANALYSIS**  
**Sub. Code : 63463**

Day and Date : Tuesday, 07 - 05 - 2019

Total Marks : 100

Time : 10.00 a.m. to 1.00 p.m.


- Instructions :
- 1) Figures to the right indicates full marks.
  - 2) All questions are compulsory.

**SECTION - I**

Q1) Solve any two.

[16]

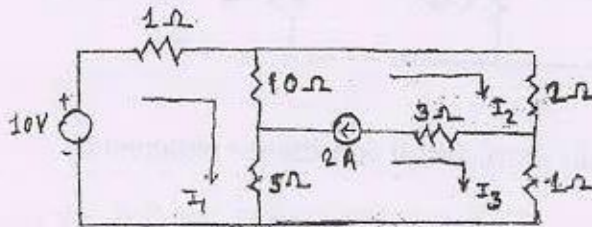- a) Determine current in  $5\Omega$  resistor for network shown in figure




- b) Write a note on tree, co-tree, twigs and links  
 c) Derive star-delta transformations.

Q2) Solve any two


[16]

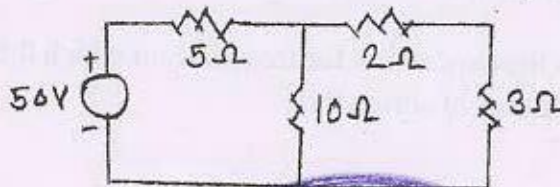- a) Use Thevenin's theorem to find the current in  $3\Omega$  resistor for the circuit shown in figure.



P.T.O.

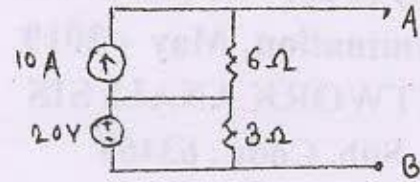- b) Replace the given network shown in figure by a single current source in parallel with a resistance.




- c) State and explain Millman's Theorem

3) Solve any two

[18]

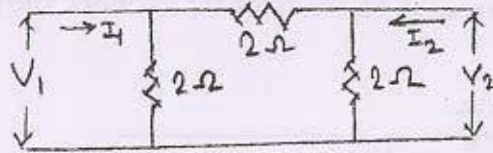- a) Derive series connection of two port network.  
b) Find ABCD-Parameter for the following Circuit



- c) Explain short circuit admittance parameter.

## SECTION - II

24) Solve any two

[18]

- a) Derive expression of resonance frequency for parallel resonance.  
b) Show that  $BW = (fr/Q)$  for series RLC. Calculate  $f_0$ ,  $f_1$  and  $f_2$  for series RLC having  $50\Omega$  resistance,  $0.2H$  inductance and  $10\mu F$  capacitance with an applied voltage of  $20V$ .  
c) Obtain the expression for frequency at which the maximum voltage across the inductor in series RLC.

[16]

25) Solve any two

- a) Design constant  $k$  type low pass filter (T and  $\pi$ -section) having design impedance of  $600\Omega$  and cutoff frequency is  $1.5kHz$ .  
b) Derive expressions of  $Z_{OT}$  and  $Z_{O\pi}$  for filters.  
c) Design  $m$ -derived high pass filter (T and  $\pi$ -section) having design impedance of  $600\Omega$  and cutoff frequencies are  $10kHz$  and  $m = 0.3$ .

26) Solve any two

[16]

- a) Explain DC voltage response for RC circuit.  
b) Write short note on sinusoidal voltage response for RL circuit.  
c) For the following Fig. 6. C capacitor has initial voltage  $V_C(-0) = 10V$  at the same instant current through inductor is zero, switch  $k$  is closed at  $t = 0$ . Find  $V(t)$  across the inductor.

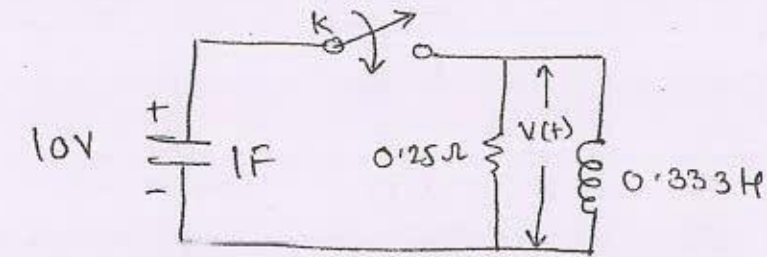


Fig. 6 C

x x x