

Seat No.

OCT-NOV 2025 WINTER EXAMINATION**1154 B.Tech. CBCS****Sub. Name: Electronics Circuit Design-II****Sub. Code: 79181/79469****Day and Date: Saturday ,06-12-2025****Total Marks: 70****Time: 10:30 AM To 01:00 PM**

- Instructions:**
1. All questions are compulsory
 2. Assume suitable data wherever necessary and mention it boldly
 3. Figures to the right indicate full marks

- Q1) Attempt following MCQ's (07*02=14) [14]**
1. Gain of an amplifier usually expressed in db because _____ [2]
 - a) It is a small unit
 - b) Calculations become easy
 - c) Human ear response is logarithmic
 - d) Gain is reduced
 2. The lower and upper cut off frequencies are also called _____ [2]

frequencies

 - a) Sideband
 - b) Half-power
 - c) Half-resonant
 - d) Resonant
 3. An LC oscillator designed to operates on _____ frequency and RC [2]

oscillators designed to operate on _____ frequency.

 - a) High, High
 - b) High, Low
 - c) Low, High
 - d) Low, Low
 4. The 7812 regulator IC provides _____ output. [2]
 - a) 5
 - b) -5
 - c) 12
 - d) -12
 5. Oscillators must use _____ feedback. [2]
 - (a) Positive
 - b) Negative
 - (c) Both a & b
 - d) none of the above

6. Find the output frequency for Astable multivibrator when $R_1 = R_2 = 2\text{K}\Omega$ and $C_1 = C_2 = 0.1\mu\text{F}$ and $R_C = 5\text{K}\Omega$ connected [2]
 a) 3.6kHz
 b) 1.4 kHz
 c) 7.5 kHz
 d) 2.4 kHz
7. State the reason for thermal shutdown of IC regulator? [2]
 a) Spikes in temperature
 b) Decrease in temperature
 c) Fluctuation in input
 d) Increase in temperature

Q2) Attempt any TWO of the following. (02*07=14) [14]

- a. Explain RC coupled Amplifier with its frequency response [7]
- b. Design a two stage RC coupled amplifier to meet the following specifications $R_s = 600\Omega$, $R_L = 2\text{K}\Omega$, frequency range is 1KHz to 100KHz, Voltage Gain per stage > 60 and supply voltage = 15V. Also calculate the overall voltage gain of the RC coupled amplifier [7]
- c. What is the need of cascading? Explain different types of coupling [7]

Q3) Attempt any TWO of the following. (02*07=14) [14]

- a. What is harmonic distortion? Explain 3 point method of calculating harmonic distortion of power amplifier. [7]
- b. Design class A Push -Pull Amplifier for following specifications: $P_o = 500\text{mW}$, loud speaker impedance = 8Ω , $V_{cc} = 12\text{V}$ [7]
- c. Design two stage voltage series feedback amplifier with overall gain at 150 and cover 3db frequency not more than 20Hz the output should be of 15Vp-p [7]

Q4) Attempt any TWO of the following. (02*07=14) [14]

- a. Draw a neat circuit diagram of astable multivibrator. Explain its operation by suitable waveforms at Base and collector [7]
- b. State and explain Barkhausen's criteria for oscillator. Also explain amplitude stability and frequency stability [7]
- c. Design power supply using LM723 for low voltage 5V [7]

Q5) Attempt any TWO of the following. (02*07=14) [14]

- a. Design Hartley Oscillator for frequency of oscillation 10MHz. Use transistor BC147. V_o (rms) = 7.5V. Assume suitable data [7]
- b. Design Schmitt Trigger for the following specifications: UTP = 3V, LTP = 1.5V, V_{cc} = 15V, $I_{c(sat)}$ = 5mA, $h_{fe(min)}$ = 40. [7]
- c. Write short note on Three terminal Adjustable Positive voltage regulator (LM 317) [7]

End Of Question Paper

Important Note for Chief Exam Officer / SRPD Coordinator / Sr Supervisor/ Student -

This Question Paper may be distributed for following Subjects as common code.

सदरची प्रश्नपत्रिका खालील विषयांकरिता वितरित करता येईल.

- 1] (101) Bachelor of Engineering (79469) Electronics Circuit Design-II Part 2 SEM 4
- 2] (1154) B.Tech. CBCS (79181) Electronics Circuit Design-II Part 2 SEM 4