

Seat No. **OCT-NOV 2025 WINTER EXAMINATION****1154 B.Tech. CBCS****Sub. Name: Network Analysis****Sub. Code: 73248/77810****Day and Date: Monday ,08-12-2025****Total Marks: 70****Time: 02:30 PM To 05:00 PM**

- Instructions:**
- 1. All questions are compulsory**
 - 2. Assume suitable data wherever necessary and mention it boldly**
 - 3. Figures to the right indicate full marks**

Q1) Attempt all MCQs.**[14]**

- i. If a graph consists of 5 nodes, then the number of twigs in the tree is?
- 1
 - 2
 - 3
 - 4
- ii. In case of ideal current sources, they have _____
- Low value of voltage
 - Zero internal resistance
 - Large value of current
 - Infinite internal resistance
- iii. In series RLC circuit bandwidth is increased by _____
- Decreasing L
 - Decreasing C
 - Increasing R
 - Decreasing R
- iv. Reciprocity Theorem is applied for _____ networks.
- Linear
 - Bilateral
 - Linear bilateral
 - Lumped
- v. The poles of driving point impedance are those frequencies corresponding to _____ Conditions.
- Short circuit
 - Open circuit
 - Voltage source
 - Resistance

vi. The relation between transmission parameter C in terms of Z parameters is _____

- A. $1/Z_{11}$
- B. Z_{11}/Z_{22}
- C. Z_{11}/Z_{21}
- D. $1+Z_{11}/Z_{22}$


vii. A Low Pass filter _____

- A. Passes high frequency to output load
- B. Passes low frequency to output load
- C. Passes only steady DC
- D. A and C Correct

Q2) Attempt any Two


a. Find the current I_x using mesh analysis.

[7]

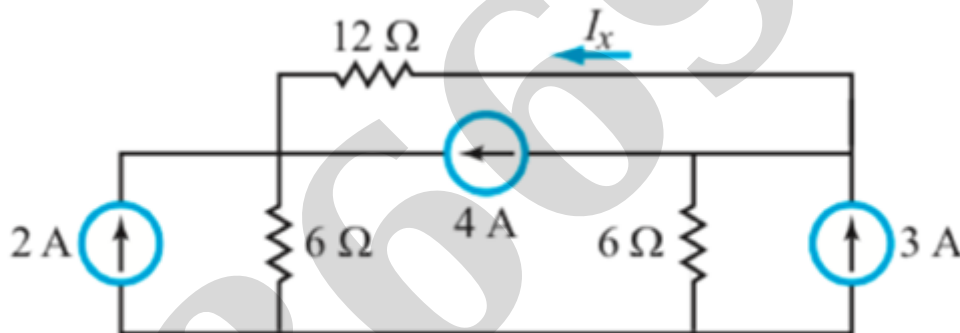


b. Find the node voltages V_x and V_y .

[7]

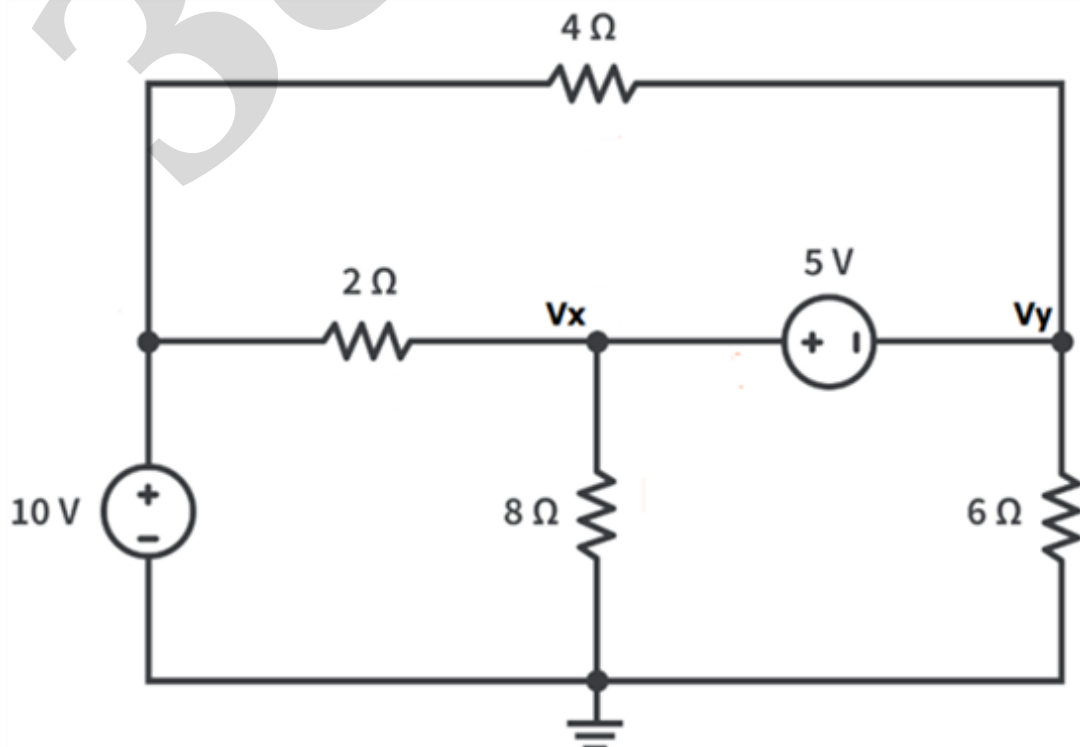


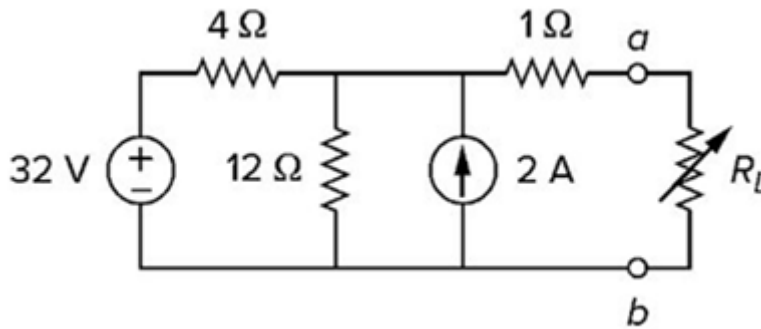- c. Find the Thevenin's equivalent of the circuit shown below across terminals a-b. [7]
Then find the current through $R_L = 6\Omega$.



Q3) Attempt any Two.

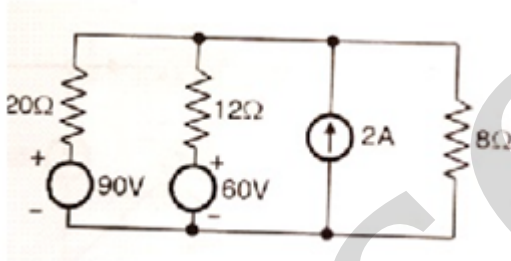
- a. Using Superposition Theorem find the current flowing through 20Ω resistance. [7]



- b. For the RLC series circuit, $C=5\mu F$, $L=2mH$, $R=2\Omega$. [7]
Find, i) Resonant frequency ii) Quality factor iii) Bandwidth.
- c. Discuss the relationship between Z , X_C , and X_L with frequency for series RLC circuit. [7]

Q4) Attempt any Two.

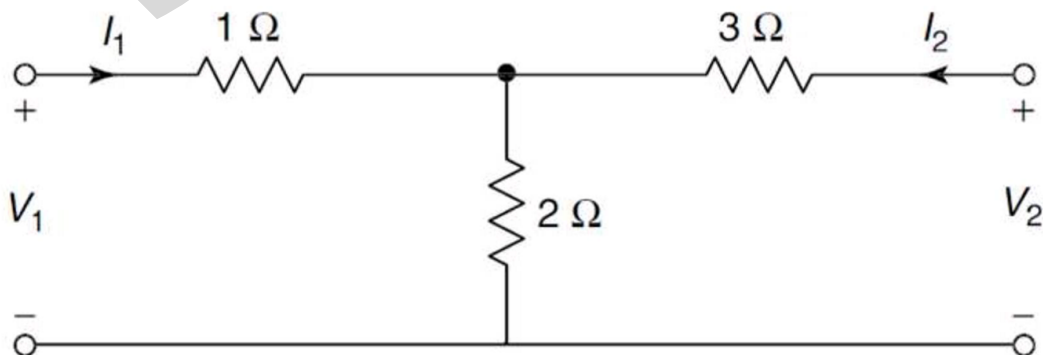
- a. Find Y-Parameters of the given network. [7]



- b. Obtain Z-Parameters in terms of Y-Parameter and vice-versa. [7]
- c. Obtain DC response of series RC circuit. [7]

Q5) Attempt any Two

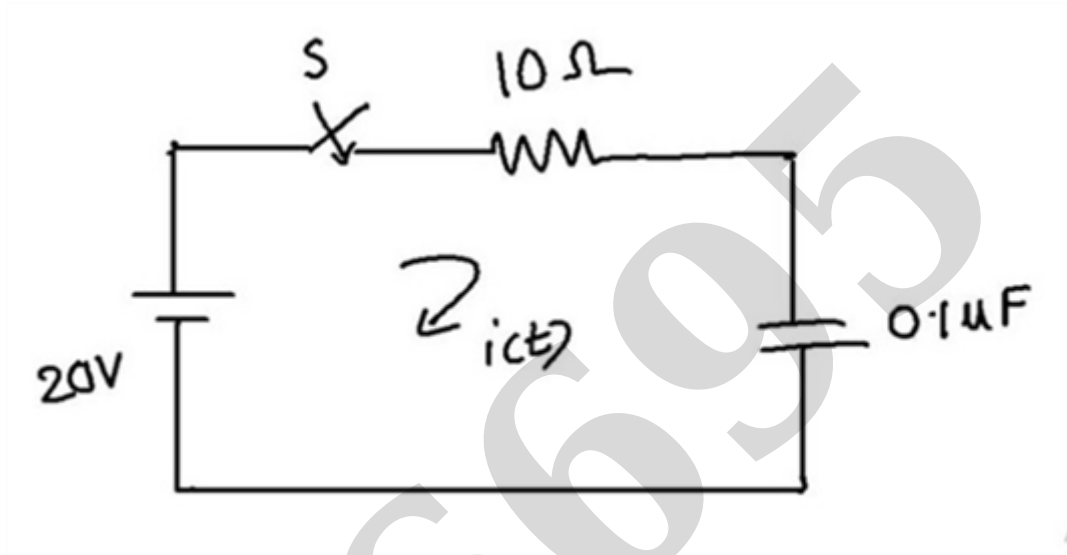- a. Design constant K- Low pass filter (both T and π section) having cut off frequency of 2 KHz to operate with terminal load resistance of 500 Ω . [7]
- b. Obtain expression for characteristic impedance Z_0 for T-Network. [7]
- c. The switch in figure is open for long time and closes at $t = 0$, determine $i(t)$ at $t > 0$. [7]



End Of Question Paper

Important Note for Chief Exam Officer / SRPD Coordinator / Sr Supervisor/ Student -

This Question Paper may be distributed for following Subjects as common code.

सदरची प्रश्नपत्रिका खालील विषयांकरिता वितरित करता येईल.

- 1] (101) Bachelor of Engineering (77810) Network Analysis Part 2 SEM 3
- 2] (1154) B.Tech. CBCS (73248) Network Analysis Part 2 SEM 3