

Seat No. **OCT-NOV 2025 WINTER EXAMINATION****11731 Bachelor of Technology (NEP-2.0)****Sub. Name: Analog Circuit Design****Sub. Code: 114444/112434****Day and Date: Thursday ,18-12-2025****Total Marks: 60****Time: 02:30 PM To 05:00 PM**

- Instructions:**
1. All questions are compulsory
  2. Assume suitable data wherever necessary and mention it boldly
  3. Draw neat labelled diagrams wherever necessary
  4. Figures to the right indicate full marks
  5. Use of Scientific calculator is allowed

**Special Inst.:** Use of Data Sheet is allowed

**Q1)** Solve following MCQ.

**[10]**

- i. TUF of FWR is related to \_\_\_\_
  - A. Transformer Utilization
  - B. load Resistance
  - C. Both A & B
  - D. None of the above
- ii. The Clipper Circuit used to -----
  - A. Increase Voltage
  - B. remove unwanted portion of waveform
  - C. Both of the above
  - D. All of the above
- iii. In positive feedback Phase Shift is .....
  - A. Less than 1
  - B. greater than 1
  - C. 0 or 360 Degree
  - D. None of above
- iv. In Wein bridge oscillator, Value of  $\beta$  is -----
  - A. 1/3
  - B. 56
  - C. 0
  - D. None of the above
- v. Monostable Multivibrator is also called as -----Multivibrator
  - A. One Shot
  - B. monostable circuit
  - C. Free Running
  - D. none of the above

- Q2) Attempt any TWO of the following. (2\*6=12) [12]**
- a. Design an unregulated power supply using L filter to give output 12V at load current 100 mA. Assume ripple factor  $r = 6\%$  [6]
  - b. Draw and explain Negative clamper circuits [6]
  - c. Draw & Explain Hybrid equivalent model for CB amplifier. [6]
- Q3) Attempt any TWO of the following. (2\*7=14) [14]**
- a. Why feedback is necessary? With help of expressions explain advantages of negative feedback. [7]
  - b. Design RC Phase shift oscillator for following specifications-  $V_{CC}=10\text{ V}$ ,  $f_{osc}=1\text{ kHz}$ ,  $h_{fe}=200/300$ ,  $h_{ie}=4.5\text{ k}$ ,  $I_C(\text{max})=200\text{ mA}$ ,  $P_D(\text{max})=250\text{ mW}$ ,  $s=10$ . [7]
  - c. Design Astable multivibrator for 5KHz frequency, duty cycle = 50%,  $V_{BE}(\text{sat})=0.7\text{ V}$ ,  $V_{CC}=12\text{ V}$ ,  $I_C(\text{sat})=10\text{ mA}$ ,  $V_{CE}(\text{sat})=0.3\text{ V}$ ,  $h_{fe}(\text{min})=100$  and  $OF=2$ . Assume suitable data if necessary. [7]
- Q4) Attempt any TWO of the following. (2\*7=14) [14]**
- a. Derive expressions for  $A_v$ ,  $A_i$ ,  $R_i$ ,  $R_o$  for Current series feedback amplifier [7]
  - b. Design a Colpitt oscillator for  $f_o=10\text{ MHz}$ ,  $V_{CC}=10\text{ V}$ ,  $R_L=2\text{ k}\Omega$ ,  $R_s=600\text{ ohm}$ ,  $h_{ie}=4.5$ ,  $R_{FC}=0.6\text{ H}$ . [7]
  - c. Explain switching parameters of transistors. [7]
- Q5) Attempt any TWO of the following. (2\*5=10) [10]**
- a. Write note on Voltage Shunt feedback topology. [5]
  - b. Draw a neat circuit diagram of monostable multivibrator. Explain its operation by suitable waveforms at Base and collector. [5]
  - c. What is Oscillator? State and explain Barkhausen's criteria for oscillator. [5]

## End Of Question Paper

**Important Note for Chief Exam Officer / SRPD Coordinator / Sr Supervisor/ Student -**

This Question Paper may be distributed for following Subjects as common code.

सदरची प्रश्नपत्रिका खालील विषयांकरिता वितरित करता येईल.

1] (1154) B.Tech. CBCS (114444) Analog Circuit Design Part 2 SEM 3

2] (11731) Bachelor of Technology (NEP-2.0) (112434) Analog Circuit Design Part 2 SEM 3

362641